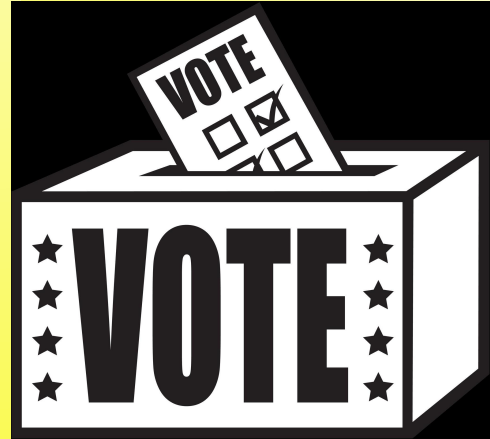


SMART VOTING SYSTEM



EEE283L

Group Members


Souvik Barman Ratul - 24121205
Faiyaz Hasin Reza-24121374
Abid Muhammad Elhan-24115001
Golam Murtaza-23121017

Mission & Goal


**Automated
Voting**



**Executive
Team**

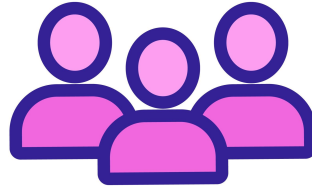


**Precision
Timing**

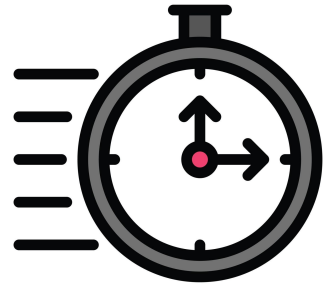


System Components

- Counter ICs (74161)
- Comparator ICs (7485)
- Logic Gate ICs (AND, OR, NOT)
- Logic toggle, probes
- 7-Segment Displays
- LED
- Push buttons and Toggles
- Jumper wires
- Digital Clock Source
- Proteus Professional 8 Software


Circuit Diagram

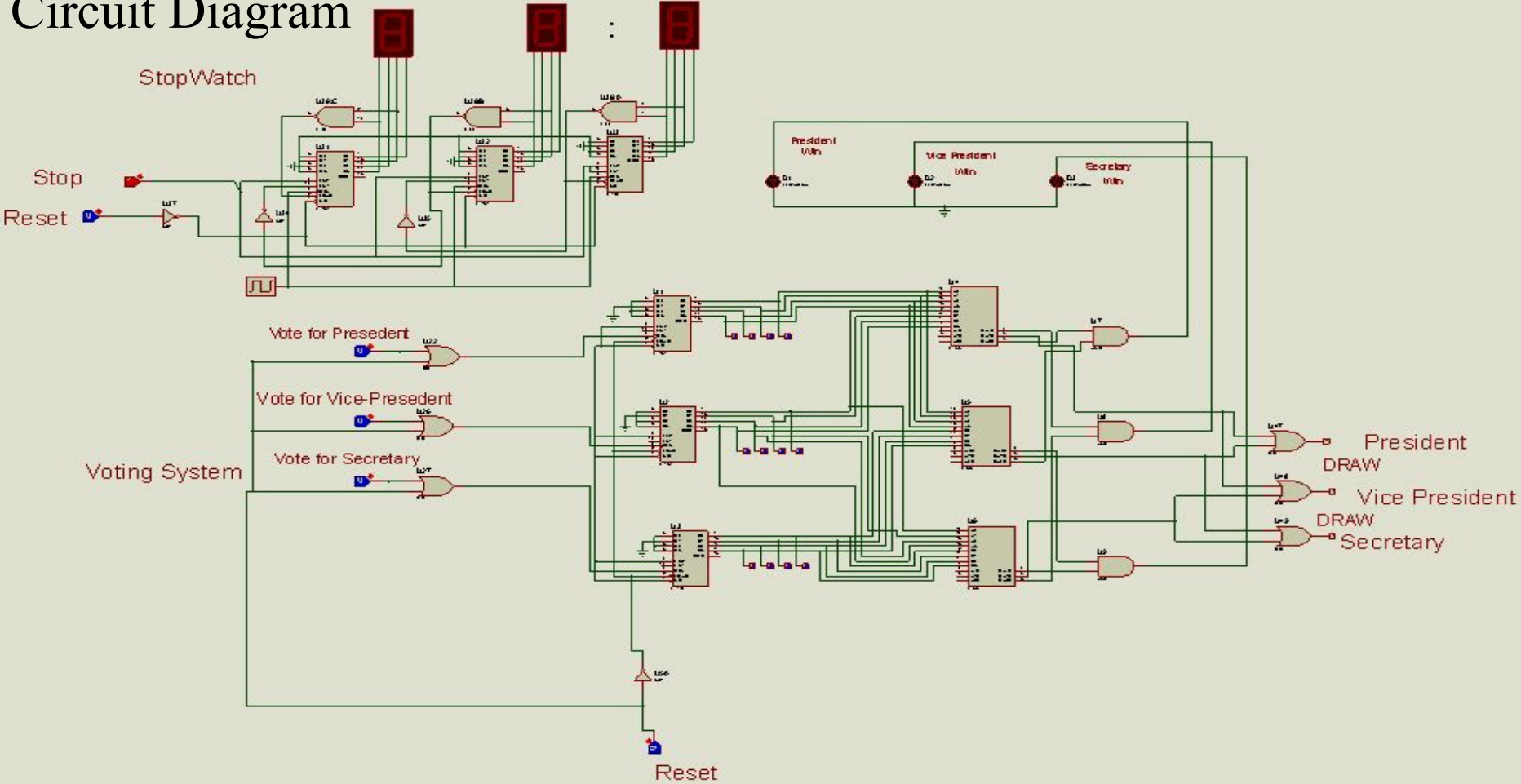


Voting Sub System

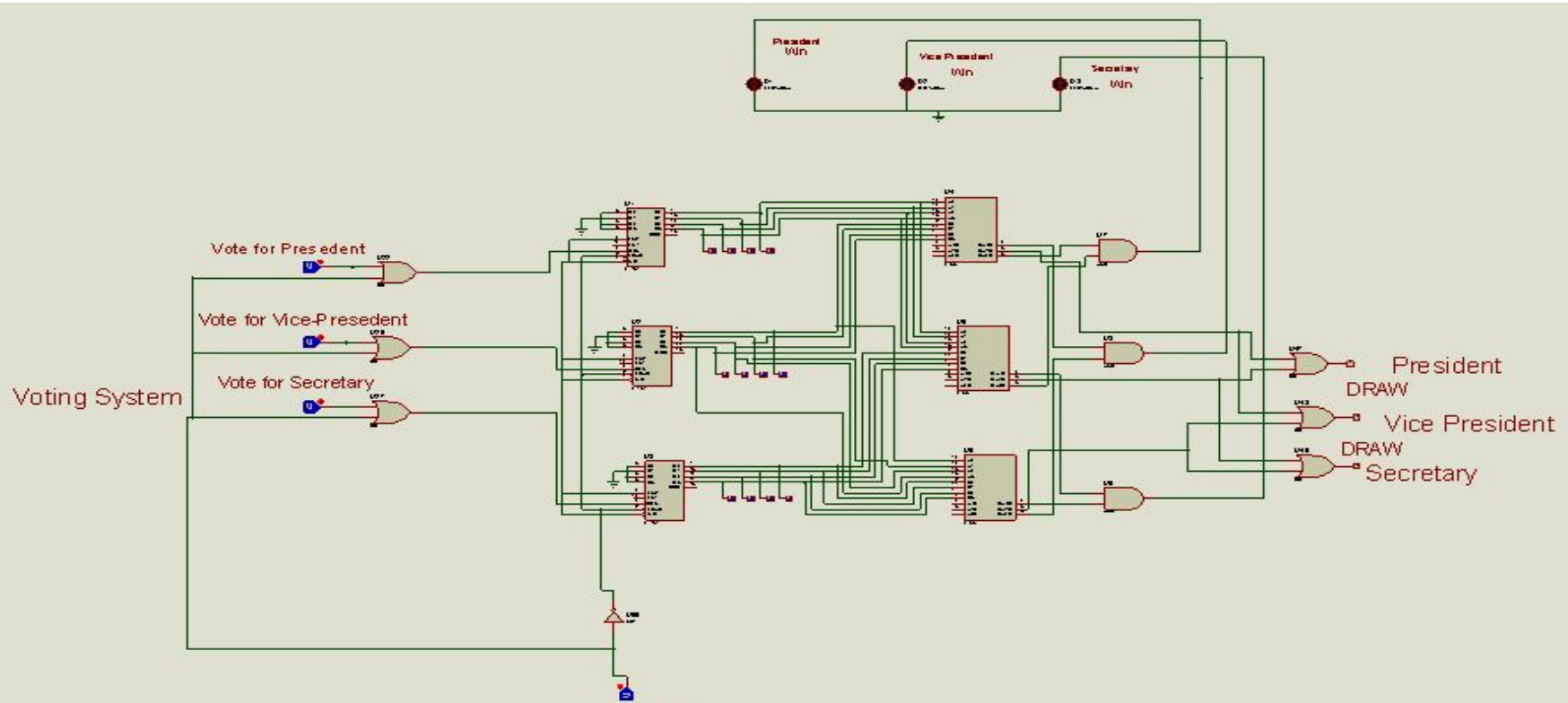

Counter Part

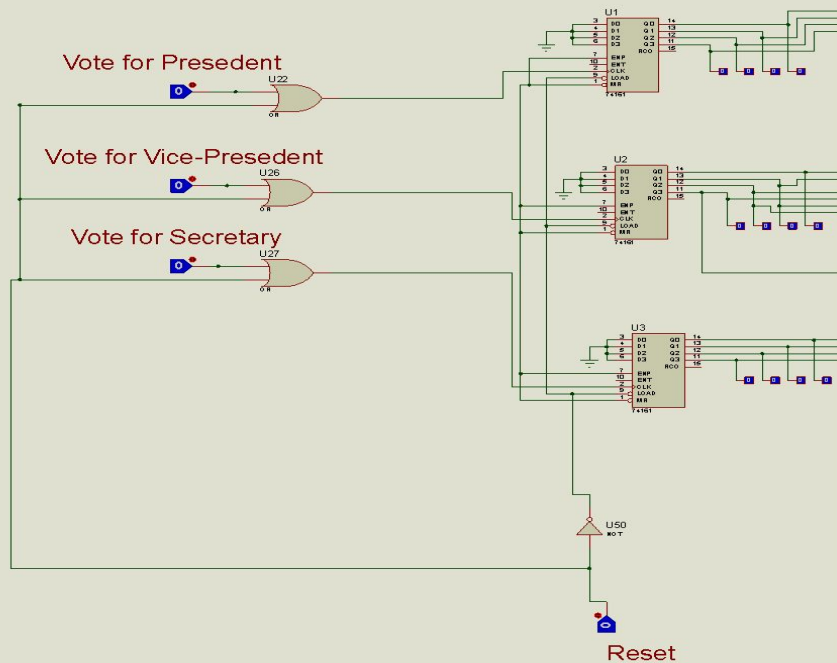

Comparator Part

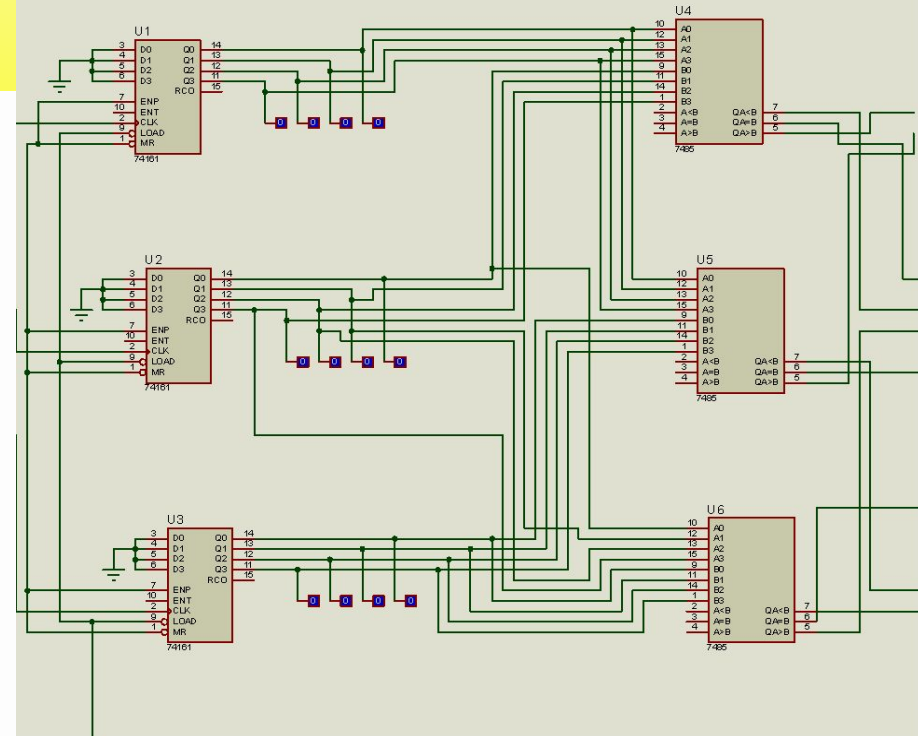


Conditions


A>B	A=B	A<B	B>C	B=C	B<C	Winner
1	0	0	1	0	0	A
1	0	0	0	1	0	A
0	0	1	1	0	0	B
0	0	1	0	0	1	C
0	1	0	0	1	0	Draw (A=B=C)
1	0	0	0	0	1	A
0	0	1	0	1	0	Draw (B = C)
0	1	0	1	0	0	Draw (A = B)

- If $A > B$ and $A > C \rightarrow A$ is winner
- If $B > A$ and $B > C \rightarrow B$ is winner
- If $C > A$ and $C > B \rightarrow C$ is winner



Output Part of Voting system

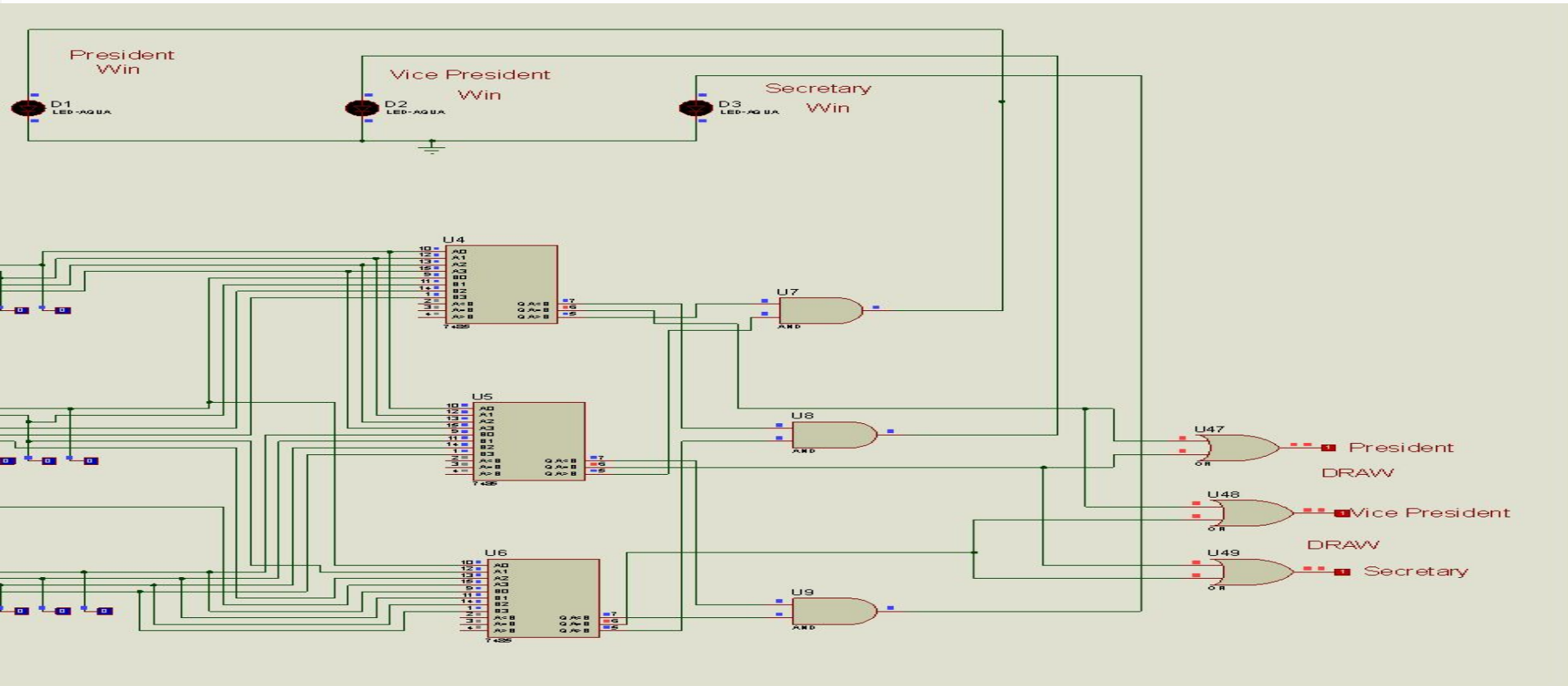

Stopwatch

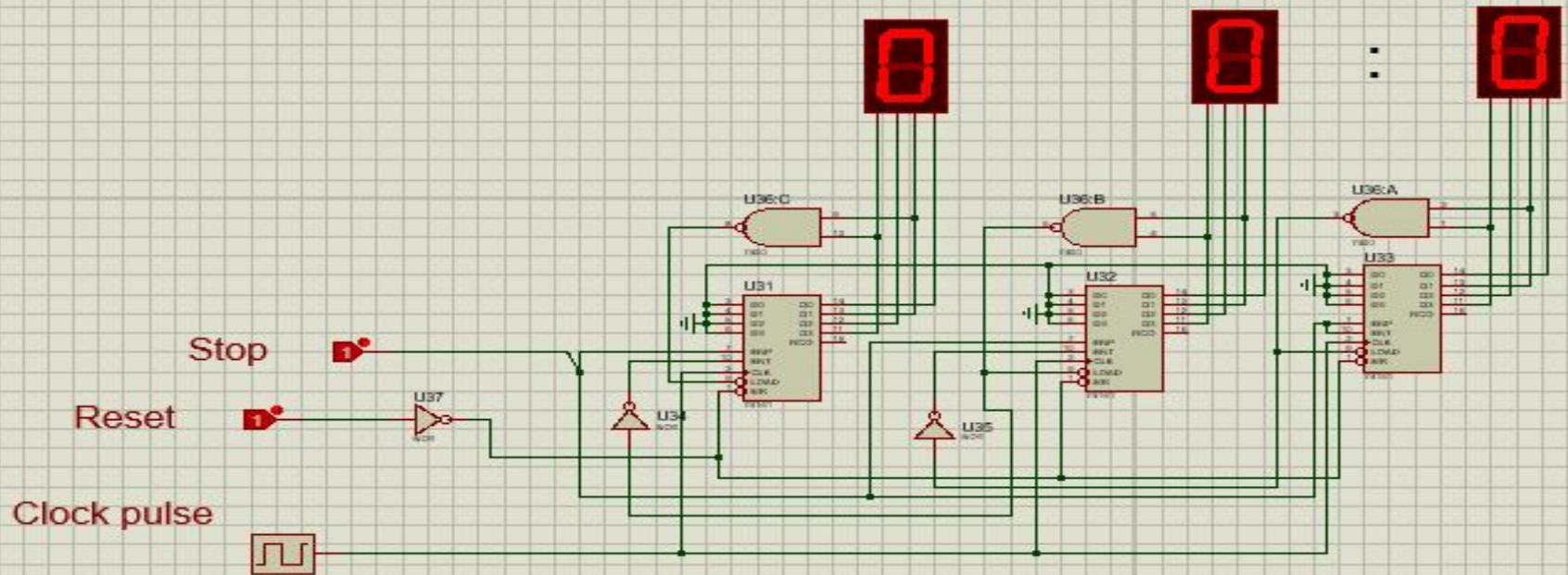


74LS161 Pinout

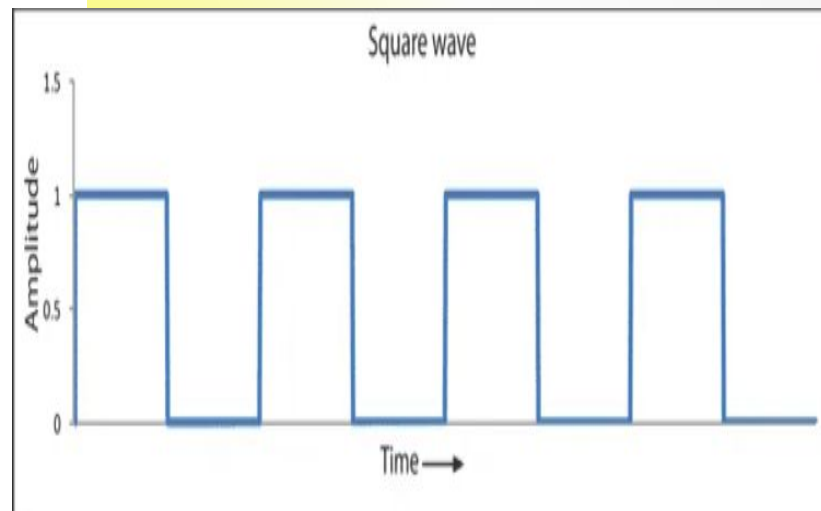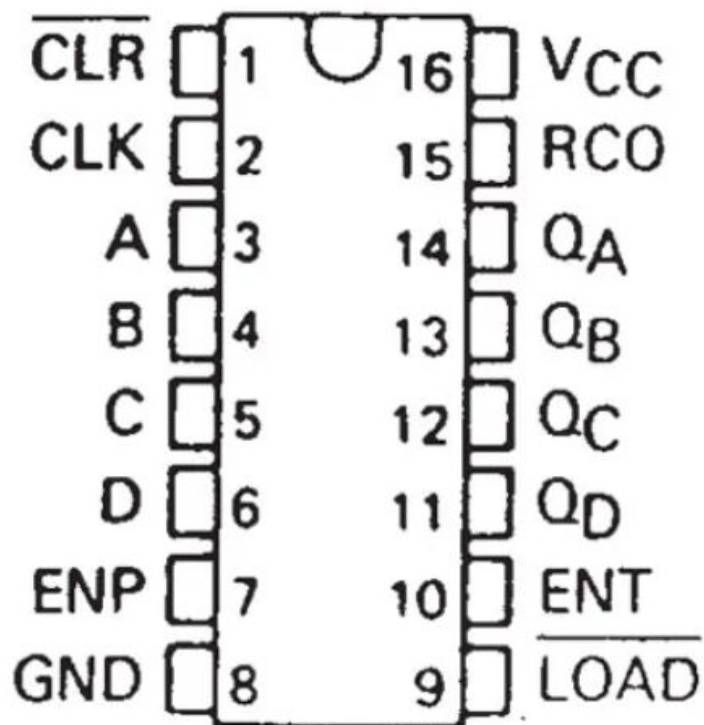


74LS47


BCD to 7-segment decoder

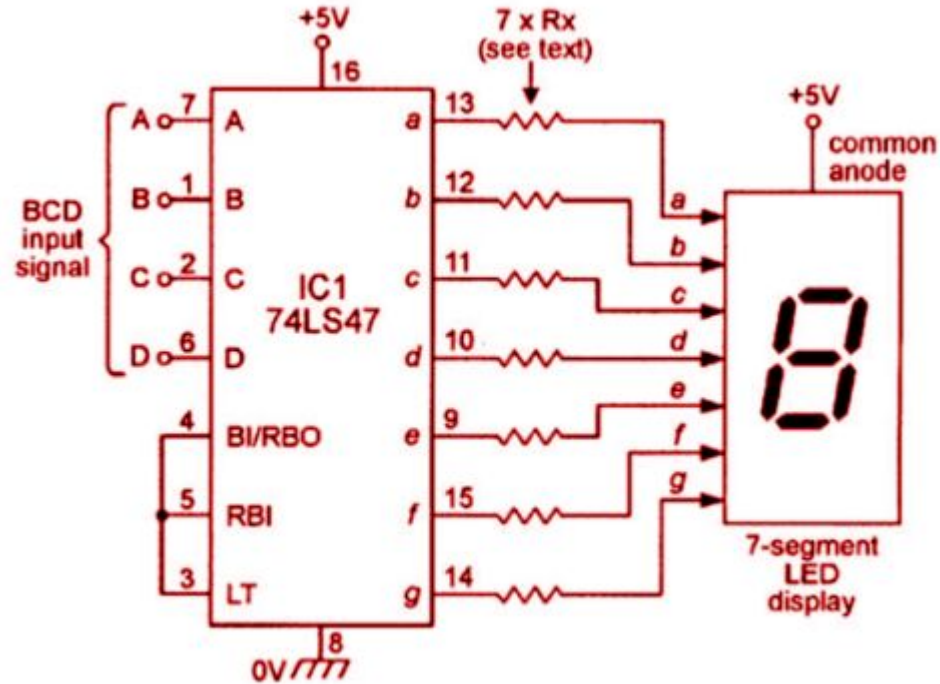

7 Segment display


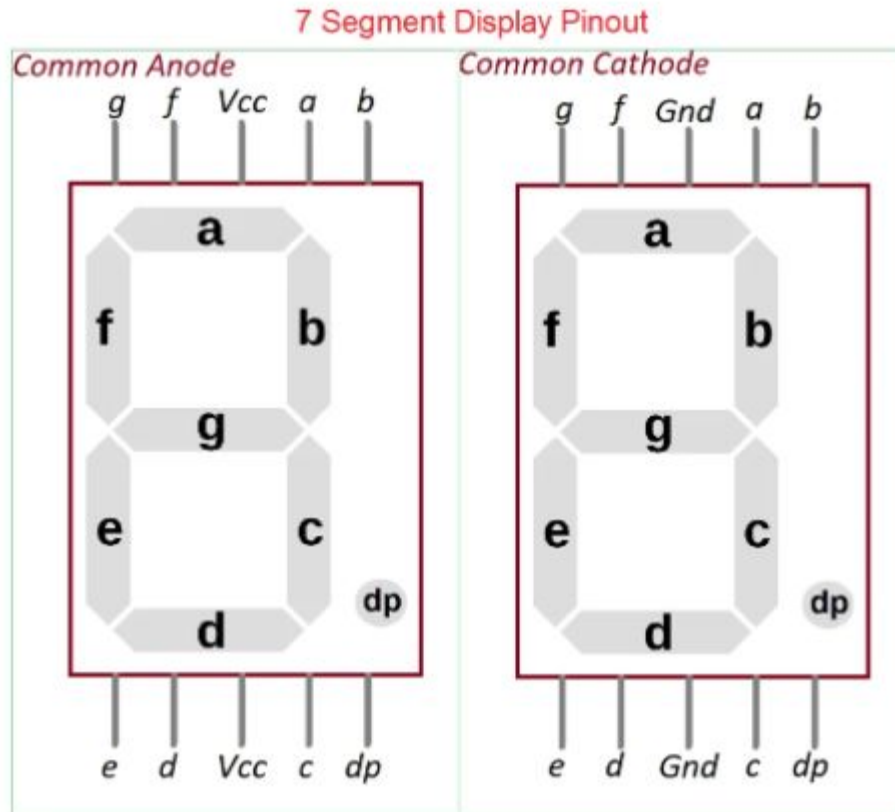


Stopwatch

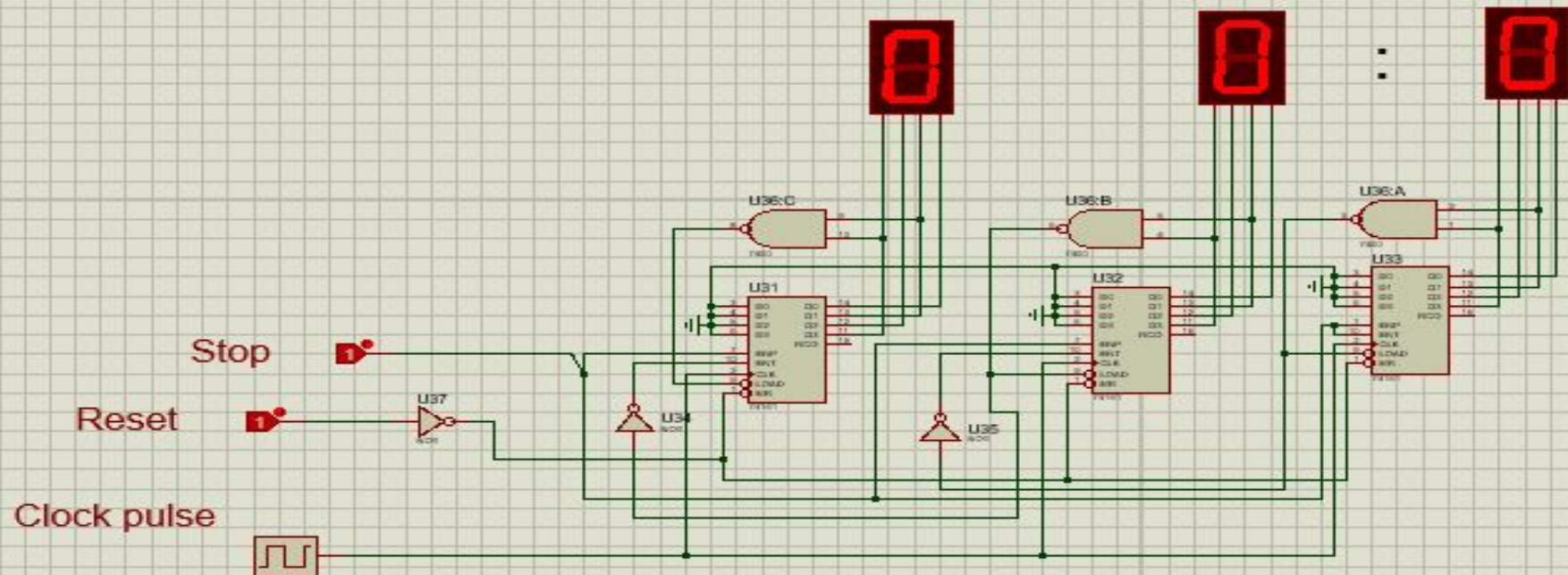


Test case 1

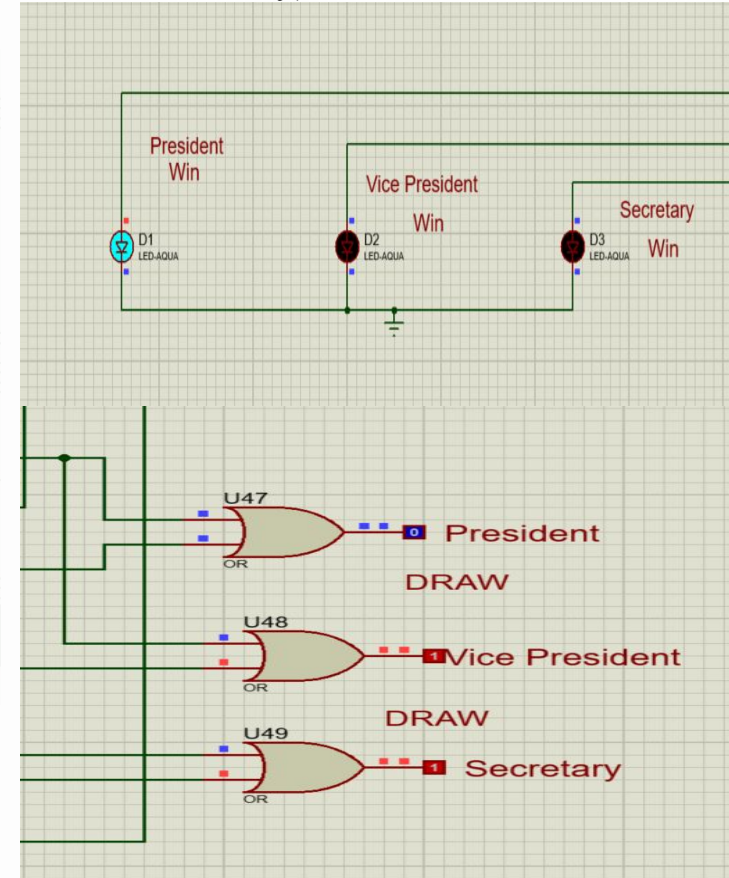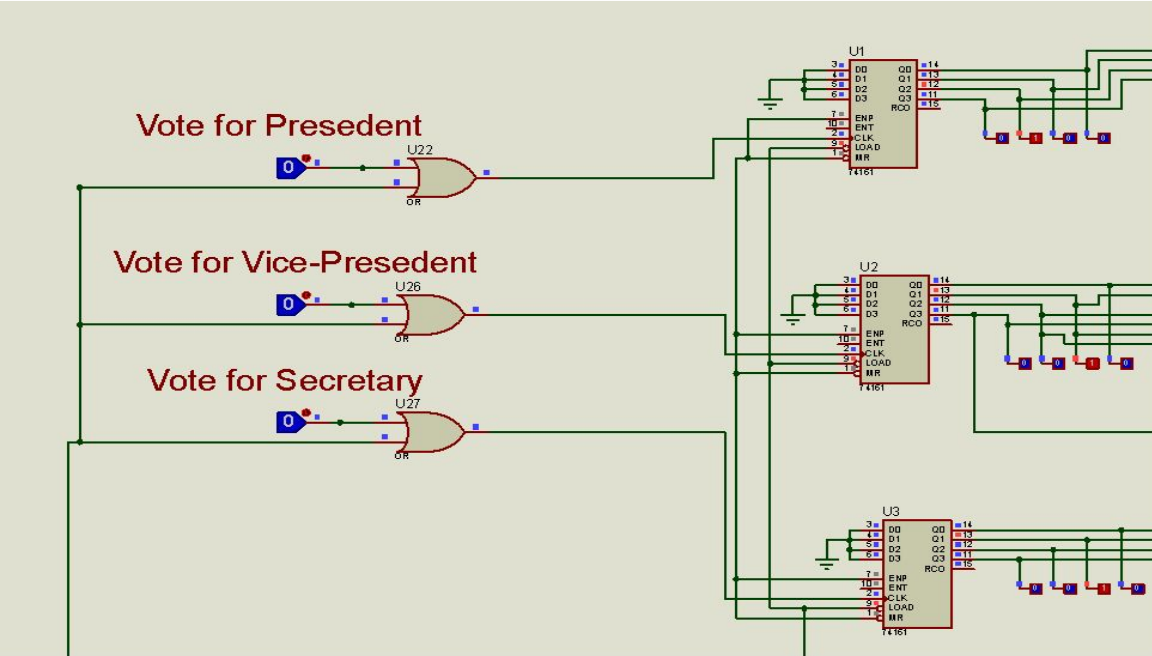For President Win & (Vice president = Secretary)



Test case 2

For contestants are draw

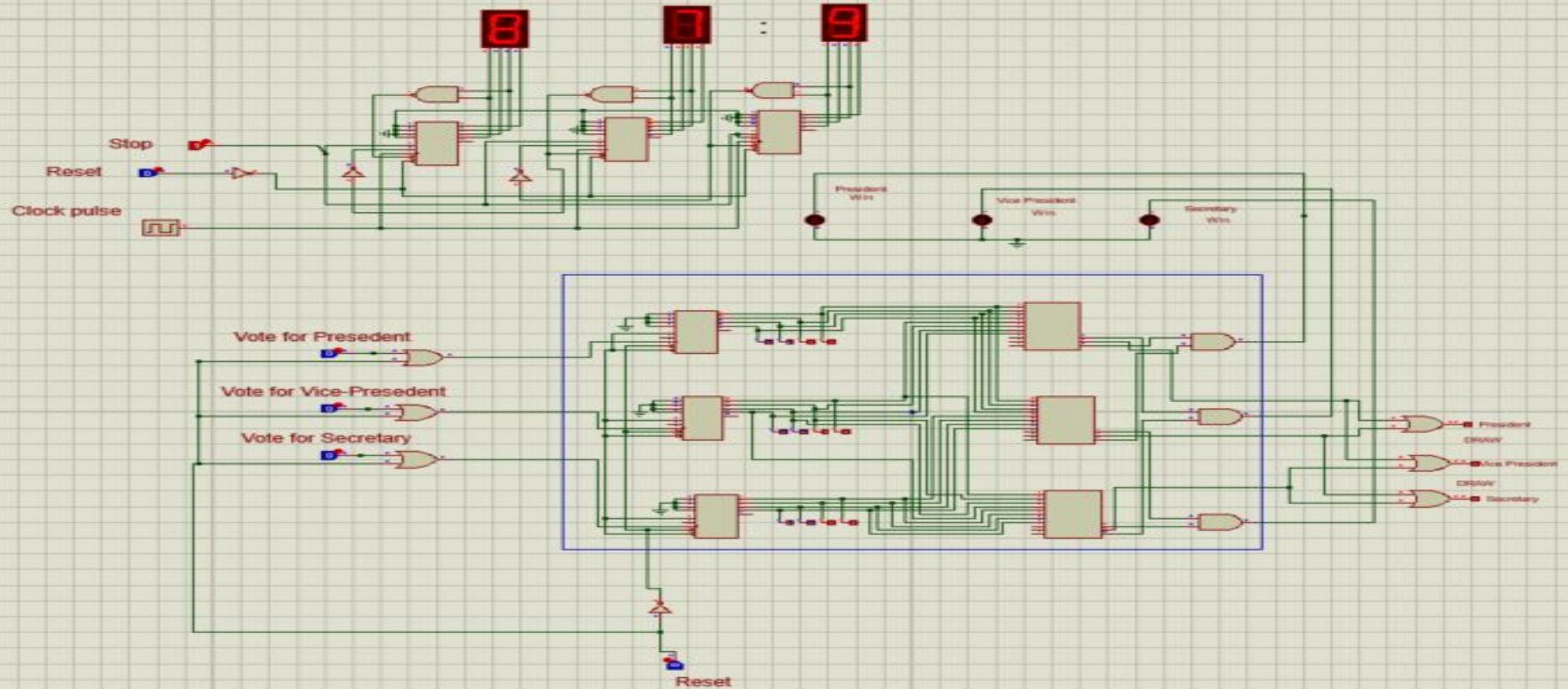

Troubleshooting

Problem 1 - Bad IC components

Problem 2 - For 7 segment display active

Problem 3 - Connection problem

Thank You